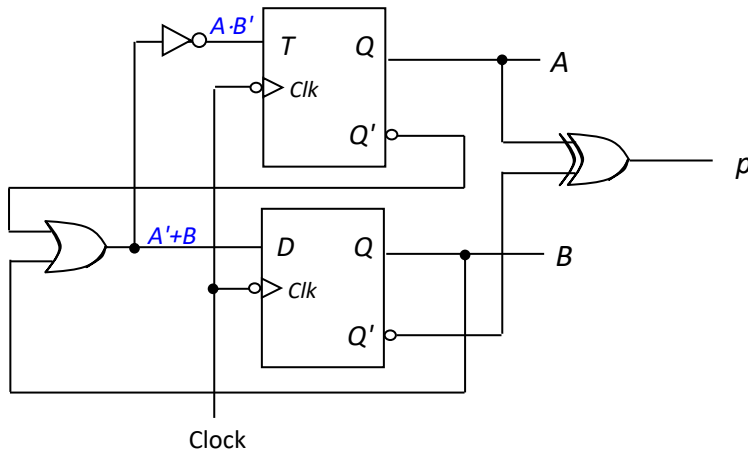


CS2100 Computer Organisation
Tutorial #9: Sequential Circuits
 (Week 11: 1 – 5 April 2024)
Answers to Selected Questions

Tutorial Questions

1. A four-state sequential circuit below consists of a **T flip-flop** and a **D flip-flop**. Analyze the circuit.



- (a) Complete the state table and hence draw the state diagram.
 - (b) Assuming that the circuit is initially at state 0, what is the final state and the outputs generated after 3 clock cycles?
- A state is called a **sink** if once the circuit enters this state, it never moves out of that state.
- (c) How many sinks are there for this circuit?
 - (d) Which is likely to be an unused state in this circuit?

Answers:


(a)

$$p = A \cdot B + A' \cdot B'$$

$$TA = A \cdot B'$$

$$DB = A' + B$$


Present state		Output <i>p</i>	Flip-flop inputs		Next state	
<i>A</i>	<i>B</i>		<i>TA</i>	<i>DB</i>	<i>A+</i>	<i>B+</i>
0	0	1	0	1	0	1
0	1	0	0	1	0	1
1	0	0	1	0	0	0
1	1	1	0	1	1	1

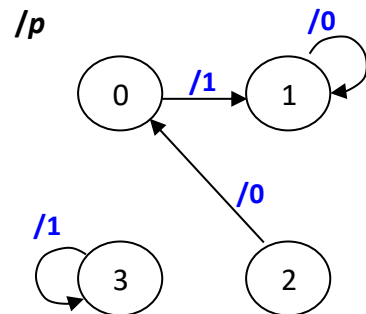


- (b) After 3 clock cycles, the circuit is in state 1, and it generated 100 as output.
- (c) There are 2 sinks: states 1 and 3.
- (d) State 3 is likely to be an unused state.

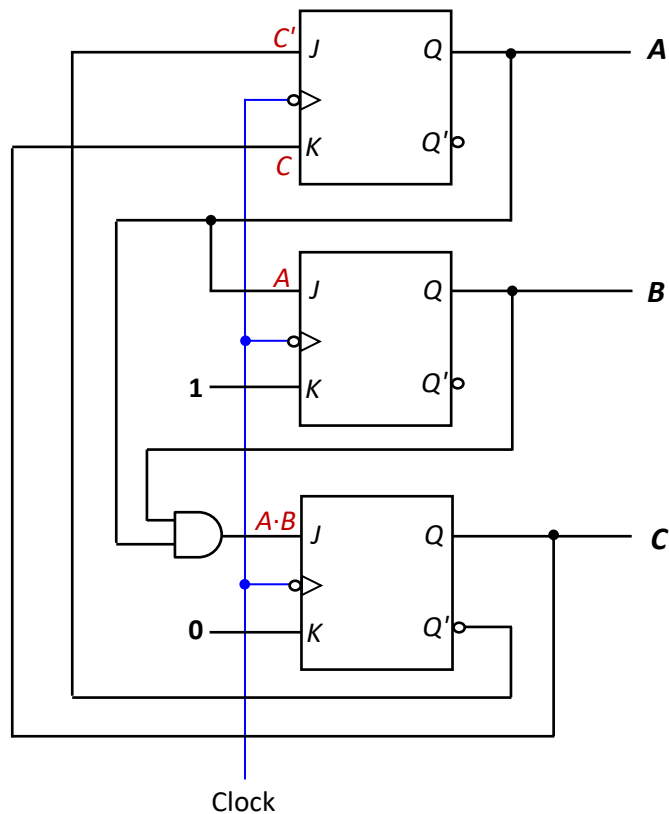2. [AY2021/22 Semester 2 Exam]

A sequential circuit with 6 states: state 1 ($ABC=001_2$) through state 6 ($ABC=110_2$) is implemented using three JK flip-flops as shown below.



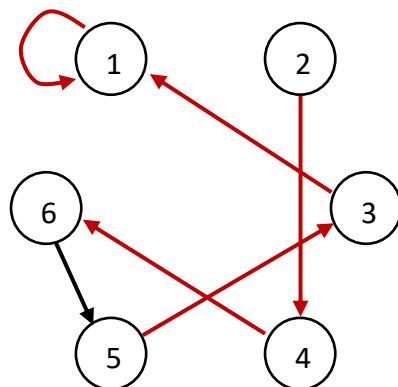(a) Complete the state diagram below. One of the transitions has been drawn for you.



(b) A circuit is **self-correcting** if for some reason the circuit enters into any unused (invalid) state, it is able to transit to a valid state after a finite number of transitions.

Is this circuit self-correcting? Explain.

Answer: Yes, it is self-correcting. State 0 transits to state 4 and state 7 transits to state 1.


Working:

(a) $JA = C'$; $KA = C$; $JB = A$; $KB = 1$; $JC = A \cdot B$; $KC = 0$.

Fill in the flip-flop inputs in the state table using the above expressions, then find the values of A^+ , B^+ , and C^+ .

Present state			Next state			Flip-flop inputs					
A	B	C	A ⁺	B ⁺	C ⁺	JA=C'	KA=C	JB=A	KB=1	JC=A·B	KC=0
0	0	0	1	0	0	1	0	0	1	0	0
0	0	1	0	0	1	0	1	0	1	0	0
0	1	0	1	0	0	1	0	0	1	0	0
0	1	1	0	0	1	0	1	0	1	0	0
1	0	0	1	1	0	1	0	1	1	0	0
1	0	1	0	1	1	0	1	1	1	0	0
1	1	0	1	0	1	1	0	1	1	1	0
1	1	1	0	0	1	0	1	1	1	1	0

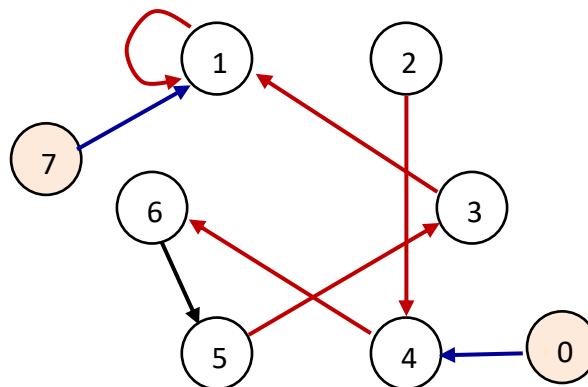State diagram with unused states 0 and 7.



3. [AY2021/22 Semester 2 Exam]

Redesign the circuit in question 2 by using only **T flip-flops**. You do not have to follow where the unused states transit to in question 2. Write out the flip-flop input functions TA , TB and TC so that your new design can be implemented with the fewest number of logic gates other than the flip-flops.

Answers: 3 logic gates (XNOR, OR, AND)




$TA = A \cdot C + A' \cdot C' = A \odot C$

$TB = A + B$

$TC = A \cdot B$


Working:

Present state			Next state			Flip-flop inputs		
A	B	C	A ⁺	B ⁺	C ⁺	TA	TB	TC
0	0	0	X	X	X	X	X	X
0	0	1	0	0	1	0	0	0
0	1	0	1	0	0	1	1	0
0	1	1	0	0	1	0	1	0
1	0	0	1	1	0	0	1	0
1	0	1	0	1	1	1	1	0
1	1	0	1	0	1	0	1	1
1	1	1	X	X	X	X	X	X

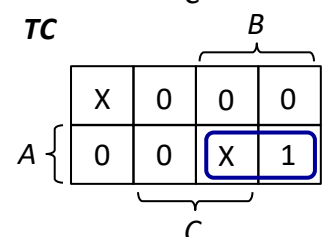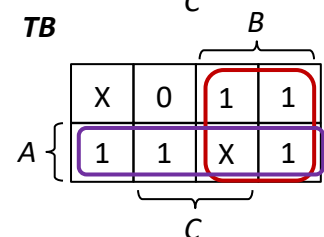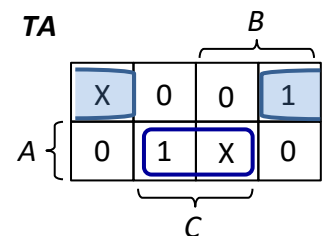

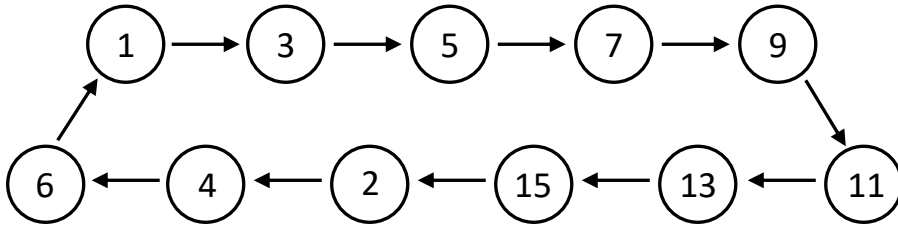4. [AY2018/19 Semester 2 exam]

A sequential circuit goes through the following states, whose state values are shown in decimal:



The states are represented by 4-bit values $ABCD$. Implement the sequential circuit using a D flip-flop for A , T flip-flops for B and C , and a JK flip-flop for D .

- (a) Write out the **simplified SOP expressions** for all the flip-flop inputs.
- (b) Implement your circuit according to your simplified SOP expressions obtained in part (a). Complete the given state diagram, by indicating the next state for each of the five unused states.
- (c) Is your circuit self-correcting? Why?

Answers:


$$DA = A \cdot B' + A \cdot C' + A' \cdot B \cdot C \cdot D$$

$$TB = C$$

$$TC = A' + B' + C'$$

$$JD = B \cdot C$$

$$KD = A \cdot B \cdot C$$

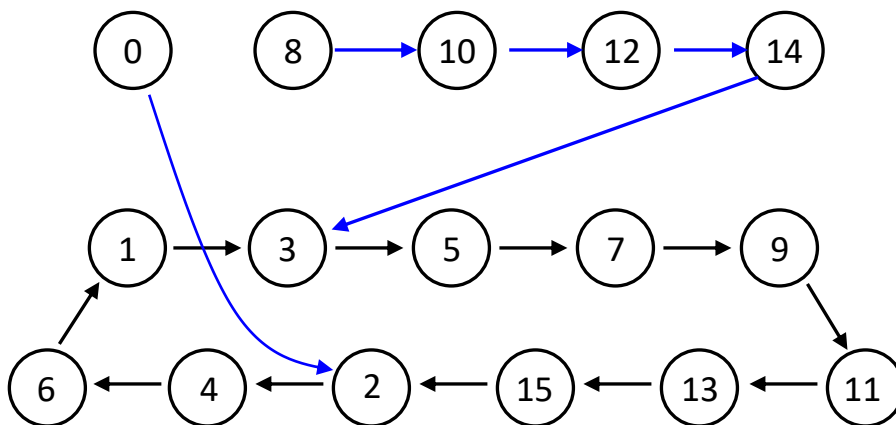

The circuit is self-correcting as any unused state can transit to a used state after a finite number of cycles.