


CS2100 Computer Organisation
Tutorial #9: Sequential Circuits
 (Week 11: 1 – 5 April 2024)

Discussion Questions:

D1. The state table on the right describes the state transition of a circuit with 4 states *A*, *B*, *C* and *D*, an input *x*, and an output *z*. For example, if the circuit is in state *A* and its input *x* is 0, then it moves into state *C* and generates the output 0 for *z*.

	<i>x</i>	
	0	1
<i>A</i>	<i>C</i> /0	<i>A</i> /1
<i>B</i>	<i>D</i> /1	<i>B</i> /0
<i>C</i>	<i>B</i> /1	<i>D</i> /0
<i>D</i>	<i>C</i> /0	<i>D</i> /0

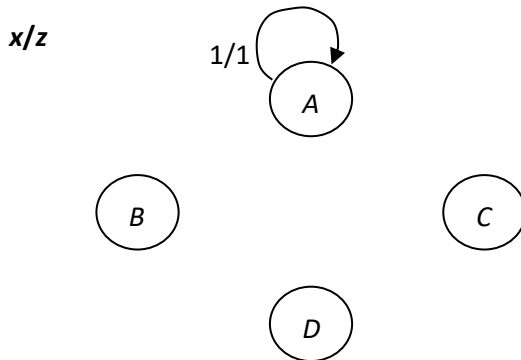
(a) Complete the state diagram below. The label of the arc indicates input/output, hence 1/1 means $x=1$ and $z=1$.




(b) Assuming that the circuit starts in state *A*, find the output sequence and state sequence for the input sequence $x = 100010$ (read from left to right). ($x = 100010$ means that initially x is 1, then in the next clock x is 0, and so on.)

D2. Match the following state diagrams to the 4 flip-flops: *JK* flip-flop, *D* flip-flop, *RS* flip-flop, and *T* flip-flop. Don't-care value is indicated by "x".


(a)

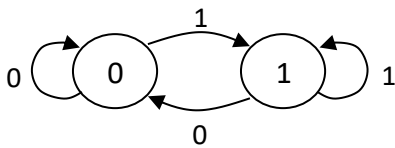


(b)

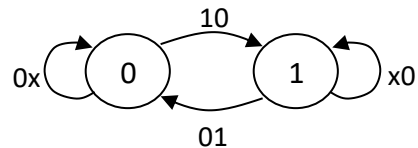

(c)

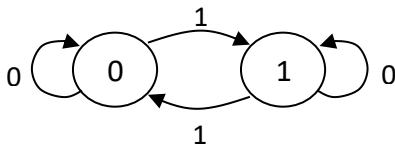


(d)

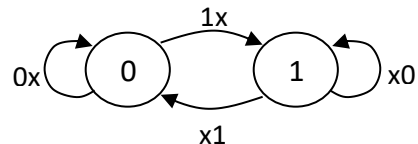

Tutorial Questions

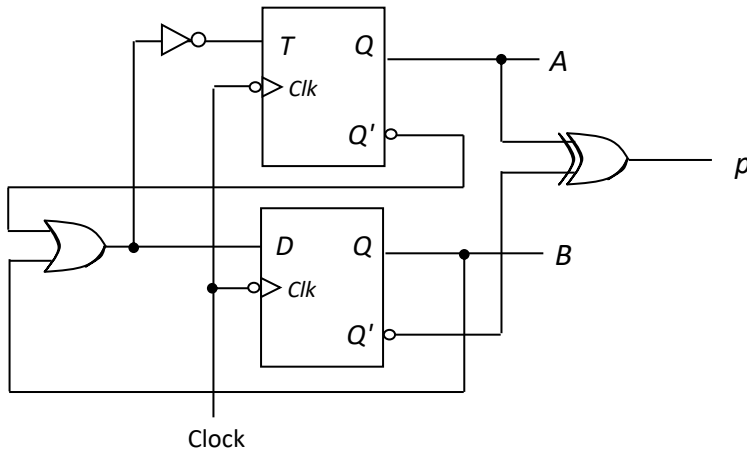1. A four-state sequential circuit below consists of a **T flip-flop** and a **D flip-flop**. Analyze the circuit.



- (a) Complete the state table and hence draw the state diagram.
- (b) Assuming that the circuit is initially at state 0, what is the final state and the outputs generated after 3 clock cycles?

A state is called a **sink** if once the circuit enters this state, it never moves out of that state.

- (c) How many sinks are there for this circuit?
- (d) Which is likely to be an unused state in this circuit?

Present state		Output <i>p</i>	Flip-flop inputs		Next state	
<i>A</i>	<i>B</i>		<i>TA</i>	<i>DB</i>	<i>A+</i>	<i>B+</i>
0	0					
0	1					
1	0					
1	1					

p

0


1

3


2

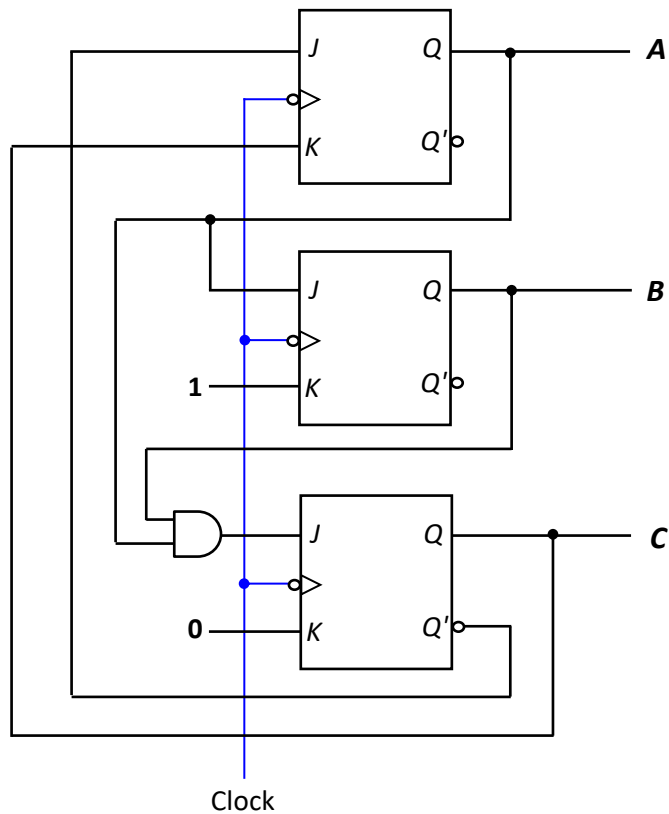2. [AY2021/22 Semester 2 Exam]

A sequential circuit with 6 states: state 1 ($ABC=001_2$) through state 6 ($ABC=110_2$) is implemented using three JK flip-flops as shown below.



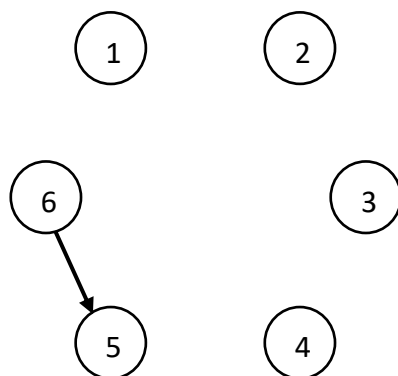(a) Complete the state diagram below. One of the transitions has been drawn for you.




(b) A circuit is **self-correcting** if for some reason the circuit enters into any unused (invalid) state, it is able to transit to a valid state after a finite number of transitions. Is this circuit self-correcting? Explain.

3. [AY2021/22 Semester 2 Exam]

Redesign the circuit in question 2 by using only **T flip-flops**. You do not have to follow where the unused states transit to in question 2. Write out the flip-flop input functions TA , TB and TC so that your new design can be implemented with the fewest number of logic gates other than the flip-flops.

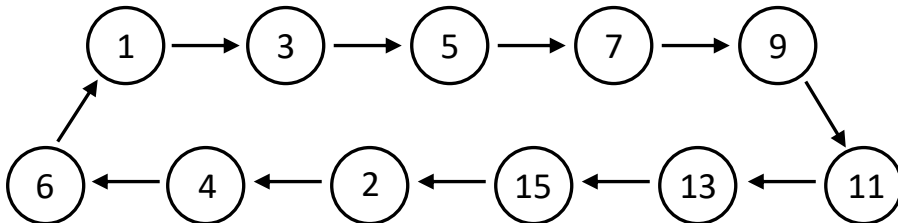4. [AY2018/19 Semester 2 exam]

A sequential circuit goes through the following states, whose state values are shown in decimal:



The states are represented by 4-bit values $ABCD$. Implement the sequential circuit using a D flip-flop for A , T flip-flops for B and C , and a JK flip-flop for D .

- (a) Write out the **simplified SOP expressions** for all the flip-flop inputs.
- (b) Implement your circuit according to your simplified SOP expressions obtained in part (a). Complete the given state diagram, by indicating the next state for each of the five unused states.
- (c) Is your circuit self-correcting? Why?

