

Digital Logic Design

Errata

- Page 6: Table 1-1. The symbol for milli- should be **m** instead of M.
- Page 40: Hamming Distance, last line in second paragraph: "... of a code by k/p " should be "... of a code by k/n ".
- Page 43: 2-19. "Which of ... in Figure 2.4?"
The correct figure should be "**Figure 2.2**".
- Page 76: Figure 4-29.
The signal for *B* in the figure on the right is incorrect. The correct diagram is shown below:

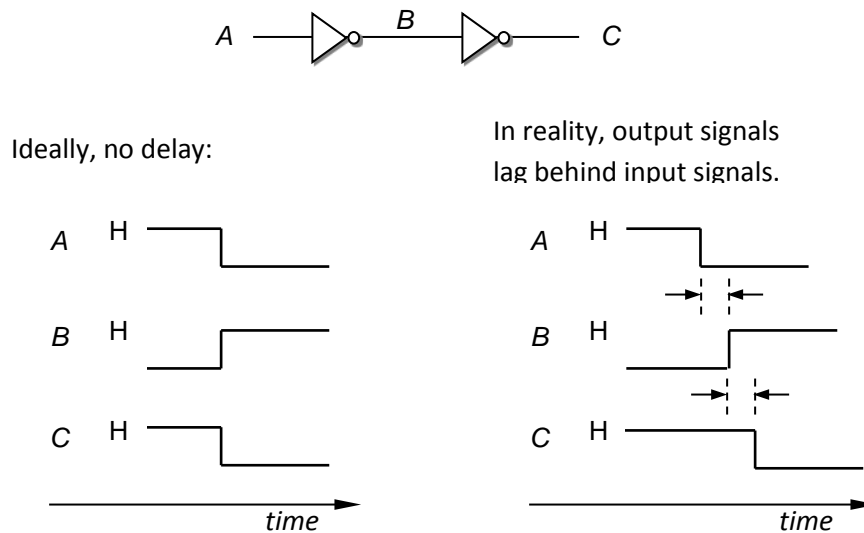


Figure 4-29 Propagation delay in a circuit.

- Page 185: Figure 8.23. Missing label "0/0" from state 0 to state 1.
- Page 240: Answer for 2-29. Smallest negative value should be **-31.75**.
- Page 242: Answer for 6-6. The truth table, expressions and circuit for *W* are wrong. Please see page 2 for correct answers.
- Page 246: Answer for 8-11. The next states for the unused states, and the state diagram are wrong. Please see page 3 for correct answers.

Chapter 6

6-6.

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	1
0	1	1	0	0	1	1	0
0	1	1	1	0	1	1	1

A	B	C	D	W	X	Y	Z
1	0	0	0	0	0	0	0
1	0	0	1	1	1	1	1
1	0	1	0	1	1	1	0
1	0	1	1	1	1	0	1
1	1	0	0	1	1	0	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	1	0
1	1	1	1	1	0	0	1

$$W = A \cdot B + A \cdot C + A \cdot D$$

$$; W = A \cdot (B + C + D)$$

$$X = A' \cdot B + B \cdot C \cdot D' + A \cdot B' \cdot C + A \cdot B' \cdot D$$




$$; X = (A + B) \cdot (B + C + D) \cdot (A' + B' + C') \cdot (A' + B' + D')$$

$$Y = A' \cdot C + C \cdot D' + A \cdot C' \cdot D$$

$$; Y = (A + C) \cdot (C + D) \cdot (A' + C' + D')$$

$$Z = D$$

$$; Z = D$$

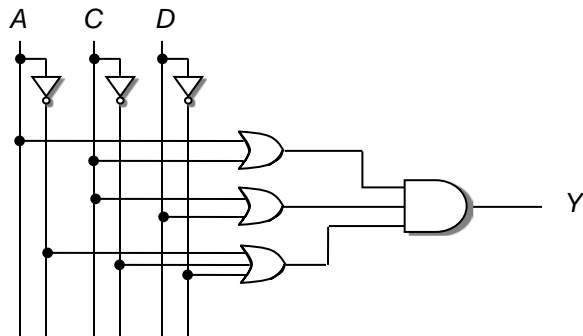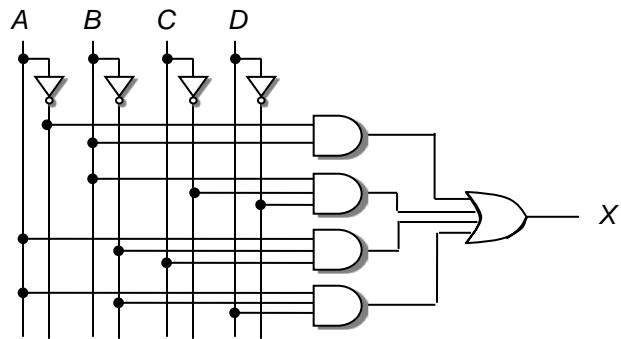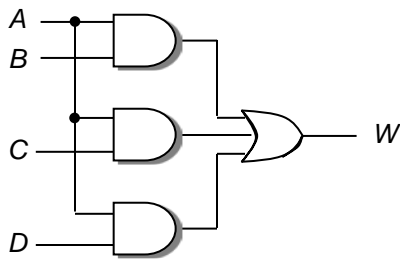

Chapter 8

8-11. $TA = A \cdot B + B \cdot C$ or $A \cdot B + A' \cdot C$

$$TB = C$$

$$TC = A' + B'$$

The following are the next states for the unused states:

$$000 \rightarrow 001$$

$$001 \rightarrow 010 \text{ or } 110$$

$$111 \rightarrow 001$$

The circuit is self-correcting.

Present state			Next state			Flip-flop inputs		
A	B	C	A ⁺	B ⁺	C ⁺	TA	TB	TC
0	0	0	X	X	X	X	X	X
0	0	1	X	X	X	X	X	X
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	0	1	0	1	0	0
1	1	1	X	X	X	X	X	X

